

Exam in Circuit QED, M2 ICFP

The flux qubit

Zaki Leghtas*

31/03/2026

Documents are authorized, but not computers, tablets, phones or any device that can connect to the internet.

In this exercise we will analyze an emblematic superconducting qubit: the flux qubit. This qubit was proposed at Delft in 1999 [Mooij *et al.*, Science, vol 285 p 1035], and demonstrated in 2003 [Chiorescu *et al.*, Science, vol 299, p. 1869]. Notably, the Canadian quantum computing company D-Wave manufactures chips of thousands of flux qubits for quantum simulations [King *et al.*, Science, vol 388, p. 199]. The circuit is displayed in Fig. 1. The goal here is to analyze the circuit and compute its low-energy spectrum.

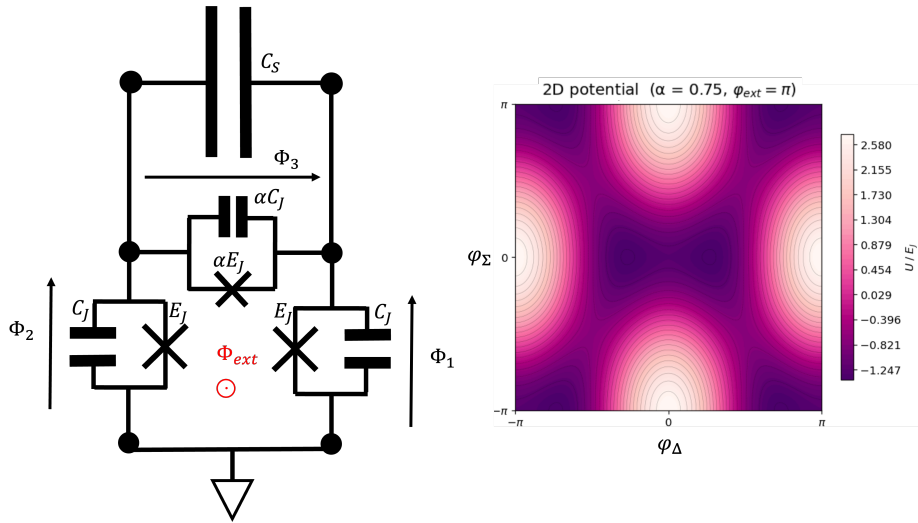


Figure 1: (Left) circuit diagram of a heavy 3-junction flux qubit. Two nominally identical Josephson junctions of energy E_J and capacitance C_J , are connected through a third junction of energy $\alpha \times E_J$ and capacitance $\alpha \times C_J$, where $0 < \alpha < 1$. The three junctions form a loop threaded by a time-independent flux Φ_{ext} . The third junction is also capacitively loaded by a large capacitor of capacitance $C_S \gg C_J$. (Right) Potential energy for $\alpha = 0.75$ and $\varphi_{\text{ext}} = \pi$.

1. Consider the circuit displayed in Fig. 1. Write down the constraint that links the degrees of freedom Φ_1, Φ_2, Φ_3 and the static external flux Φ_{ext} .
2. Compute the potential energy $U(\Phi_1, \Phi_2)$.
3. Compute the kinetic energy $T(\dot{\Phi}_1, \dot{\Phi}_2)$.
4. Express U and T in terms of the common and differential fluxes:

$$\begin{aligned}\Phi_\Sigma &= (\Phi_1 + \Phi_2)/2 \\ \Phi_\Delta &= (\Phi_1 - \Phi_2)/2.\end{aligned}$$

*zaki.leghtas@phys.ens.fr

5. We recall that the phase φ corresponding to flux Φ is defined as $\varphi = 2\pi\Phi/\Phi_0$, with Φ_0 being the superconducting flux quantum.

Show that the circuit Hamiltonian takes the form

$$\begin{aligned}\hat{H} &= 4E_{C_\Sigma}N_\Sigma^2 + 4E_{C_\Delta}N_\Delta^2 + U(\varphi_\Sigma, \varphi_\Delta) \\ U(\varphi_\Sigma, \varphi_\Delta) &= -E_J (2 \cos(\varphi_\Delta) \cos(\varphi_\Sigma) + \alpha \cos(2\varphi_\Delta - \varphi_{\text{ext}})) ,\end{aligned}$$

and derive the expressions for $E_{C_\Sigma}, E_{C_\Delta}$. Simplify these expressions in the limit $C_S \gg C_J$.

6. For the remainder of this exercise, we will focus on the bias point $\varphi_{\text{ext}} = \pi$. What are the symmetries of the potential $U(\varphi_\Sigma, \varphi_\Delta)$ (i.e. inversion symmetries, translational symmetries, mirror symmetries, etc) ?
7. In order to gain insight on the lowest eigenstates of H , we will locate the minima of the potential U . Justify that we may limit our search for potential minima along the segment $\varphi_\Sigma = 0$. For the remainder of the exercise, we will freeze $\varphi_\Sigma = 0$ and treat this as 1D problem of the variable φ_Δ .
8. What values of φ_Δ are extrema of U along the segment $\varphi_\Sigma = 0$? Verify if these extrema are minima or maxima. Separate the cases $\alpha > 1/2$ and $\alpha < 1/2$. What does crossing the value $\alpha = 1/2$ remind you of ?
9. Plot the 1D potential $\varphi_\Delta \rightarrow U(\varphi_\Sigma = 0, \varphi_\Delta)$ in the two cases $\alpha < 1/2$ and $\alpha > 1/2$. For each case, express the persistent current circulating in the loop for each potential minimum.
10. Let's first assume $\alpha \ll 1/2$ and $E_J \gg E_{C_\Delta}$. By analogy to a circuit derived in class, describe the spectrum of this circuit.
11. In the case where $\alpha > 1/2$, represent qualitatively the two lowest eigenfunctions of this circuit for "small" and "large" C_S . These generally serve as the flux qubit computational states.